

# Institute of Space Technology Islamabad

## Digital Logic Design Lab



**Title:** Design and Implementation of Adder and Subtractor.

**Date of Experiment:** 05-04-2023

**Lab number:** 08

**Names:**

Muhammad Bin Nasir	220201012
Aiza Shafqat	220201036
Muzammil Ali	220201061
Rabeesha Tanveer	220201051

## Objectives:

- To Understand and Implement Half Adder and Full Subtractor.
- To Understand and Implement Half Subtractor and Full Subtractor.
- To understand and implement 4-bit Adder.

## Equipment:

- Proteus Software

## Theory:

### **1 . Half Adder:**

A half adder is a type of digital circuit which can be used to add two bits together. It takes two inputs, and produces two outputs, one sum bit, and one carry bit.

$$0 + 0 = 0$$

$$0 + 1 = 1$$

$$1 + 0 = 1$$

$$1 + 1 = 10$$

Truth Table

Input		Output	
A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

### **2 . Full Adder:**

To add three bits, we use a full adder. It adds 3 bits together, and produces to output bit, one sum bit and one carry bit.

A	B	C	Sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

### 3 . Half Subtractor:

Like a half adder, a half subtractor can be used to perform subtraction of two bits, one bit is minuend, and one is subtrahend. It produces two outputs, one is a borrow bit and one is a difference bit.

A	B	D	B <sub>0</sub>
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0


### 4 . Full subtractor:

A full subtractor can be used to find the difference between 3 bits, where one bit is a minuend, and two bits are subtrahend.

B-in	Y	X	Diff.	B-out
0	0	0	0	0
0	0	1	1	0
0	1	0	1	1
0	1	1	0	0
1	0	0	1	1
1	0	1	0	0
1	1	0	0	1
1	1	1	1	1

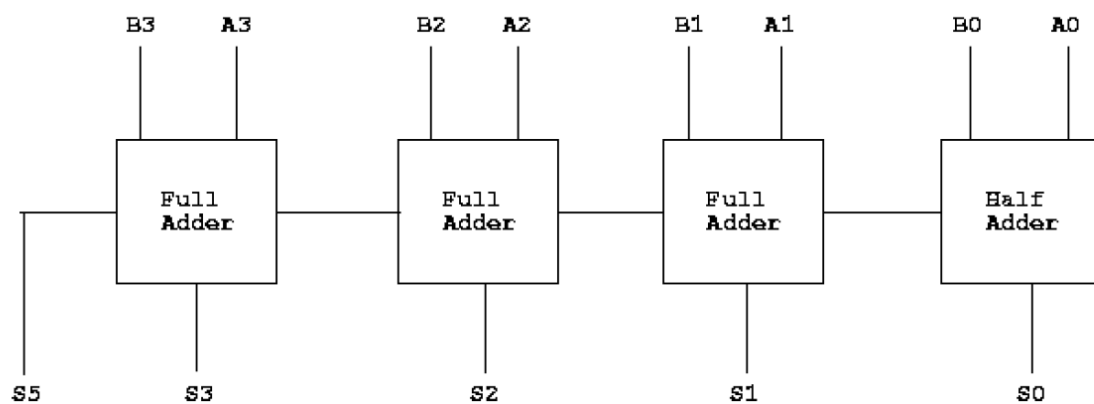
### 5 . 4 bit Adder:

We can combine N number of Full adders, to add N bits of binary. To add 4 bits of binary, we can use a combinatorial circuit of 4 full adders, or one half adder and 3 full adders. Each full adder gets the carry from previous full adder.


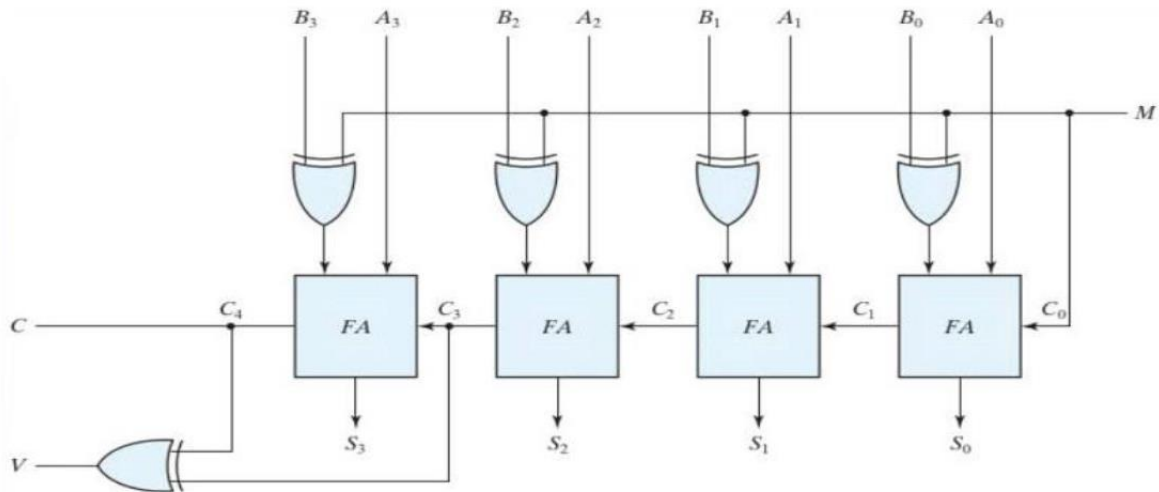
## 6 . Adder Subtractor:

An adder subtractor is a type of circuit which can be used to perform addition or subtraction based upon a control input. It is a single circuit working both as an adder and a subtractor.



### Task 1:

Implement Half Adder and Full Adder circuits.

Find out their output equation using any method and implement it. Form a truth table and verify it.

### Half Adder

## Truth Table:

Truth Table

Input		Output	
A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

## Equation:

A	B	0	1	
0				
1			1	

$\Rightarrow AB$


Carry

A	B	0	1	
0			1	
1		1		




$\Rightarrow A'B + AB' = A \oplus B$

Sum

## Circuit:

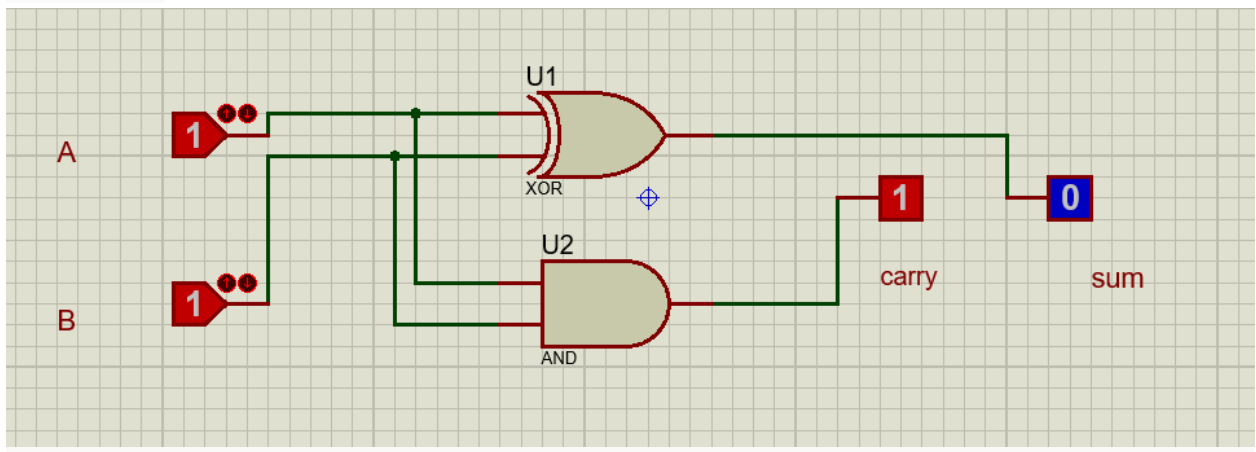

## Working:

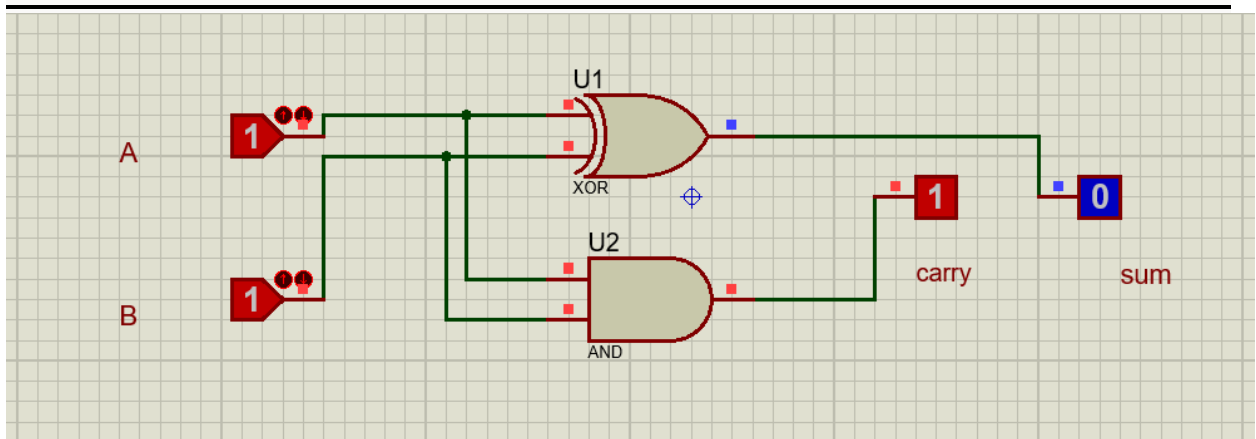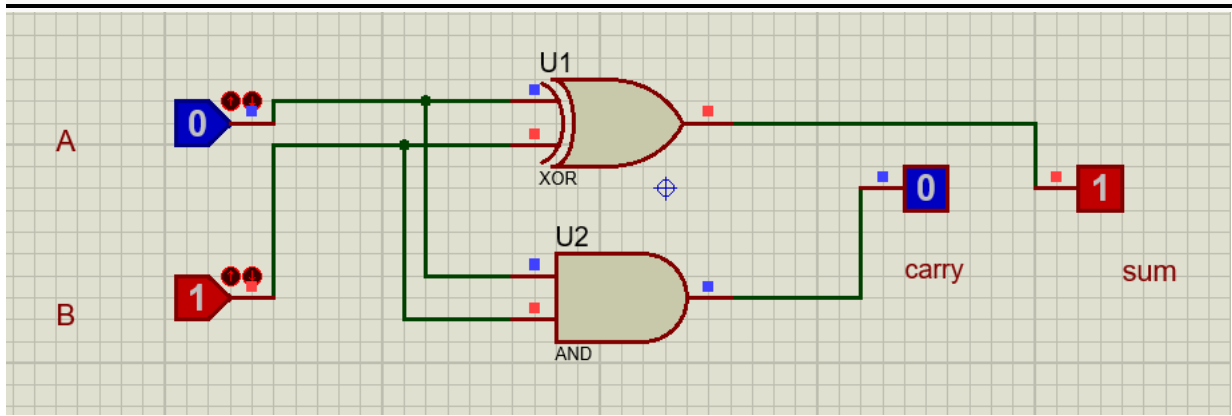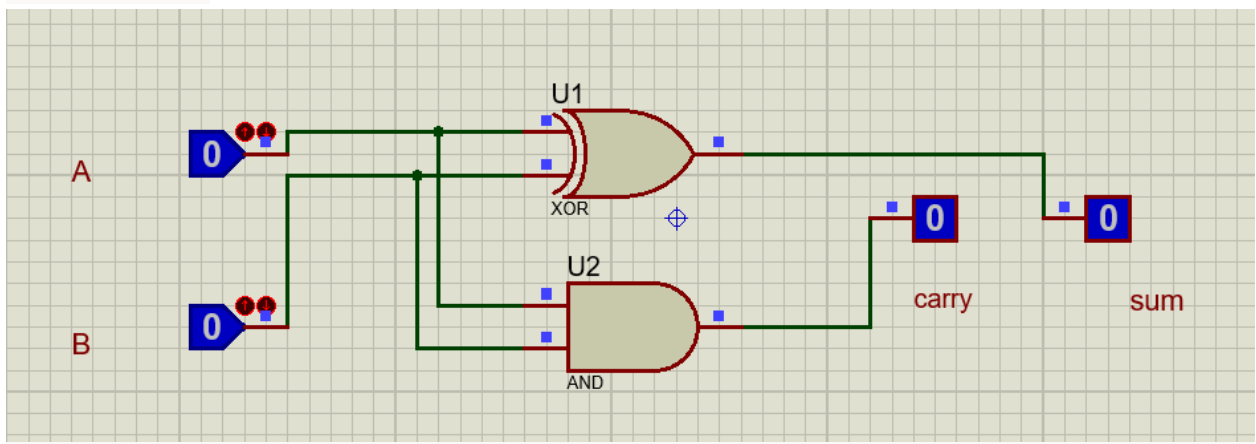


## Full Adder

### Truth Table:

A	B	C	Sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

### Equation:

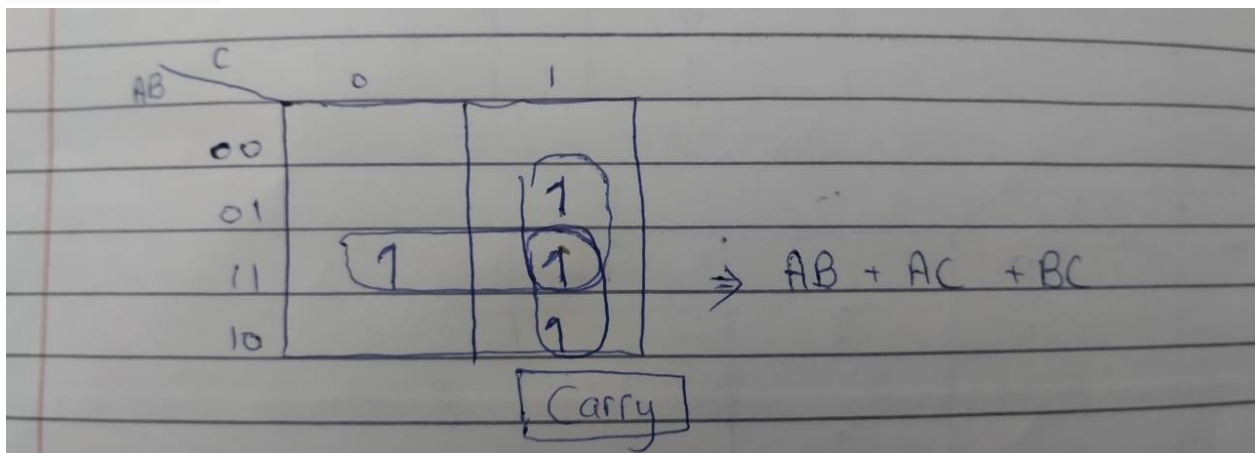




AB \ c	0	1
00	0	1
01	1	0
11	0	1
10	1	0



$\Rightarrow A'B'C + A'BC' + ABC + AB'C'$



Sum

## Circuit:

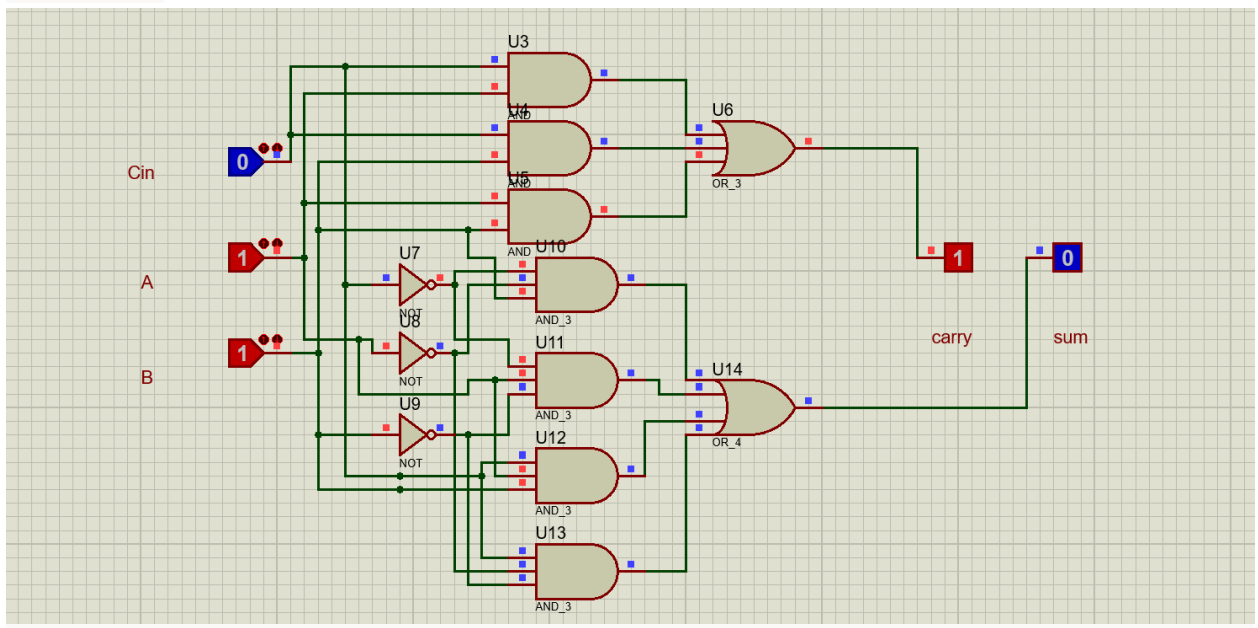

## Working:

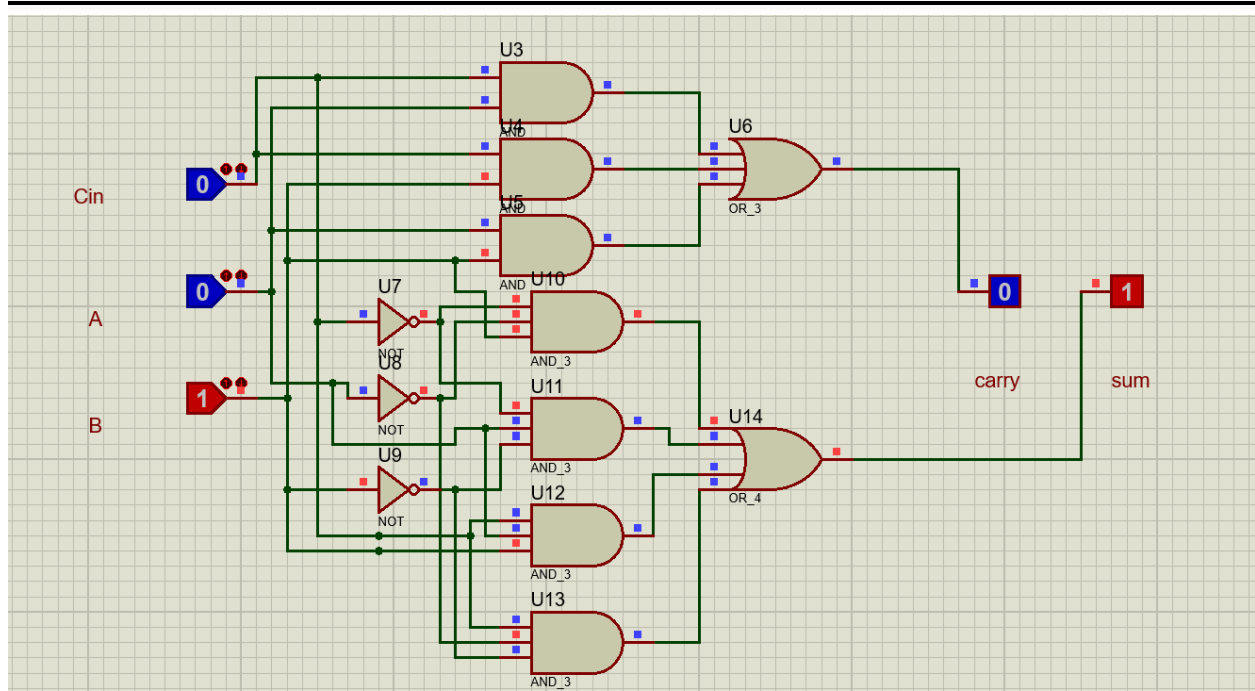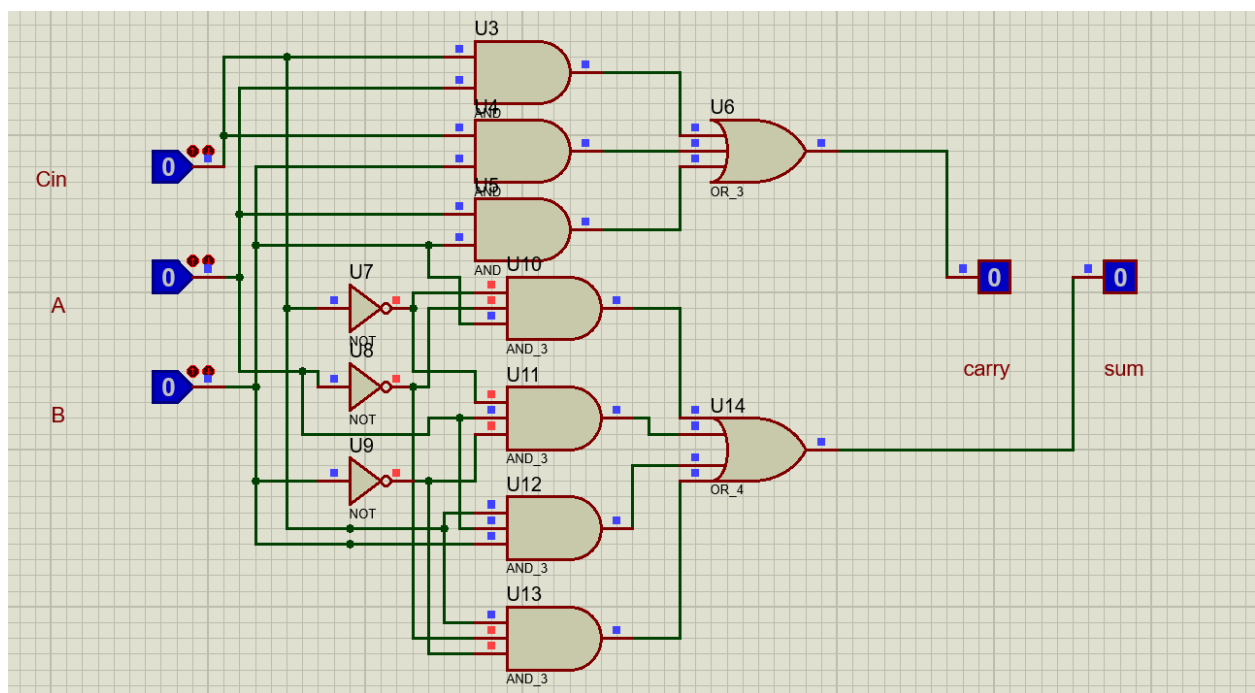

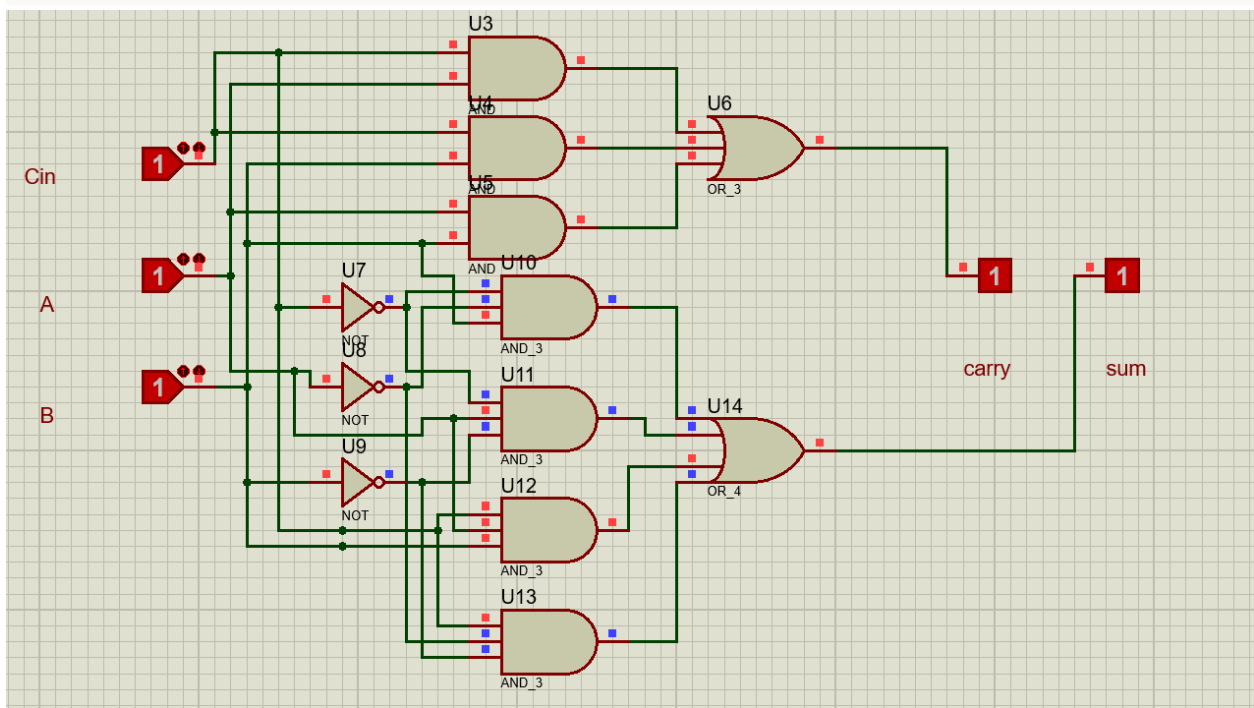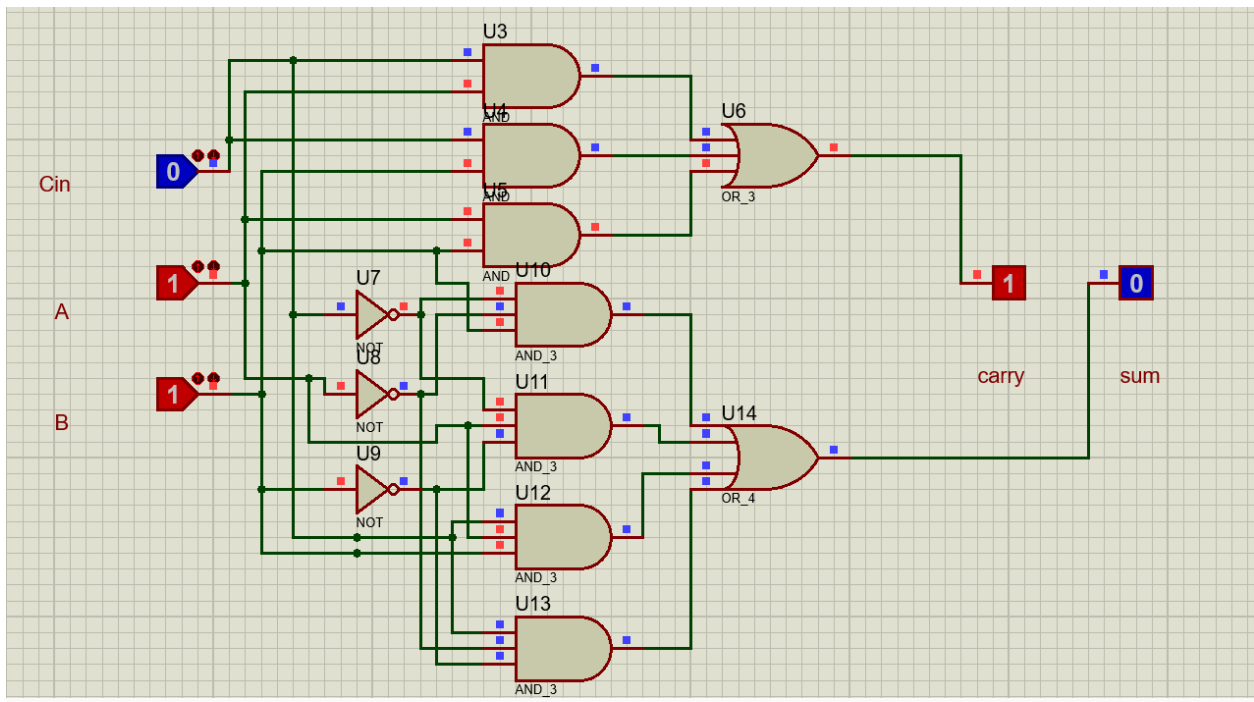

## Task 2:


Implement half subtractor and full subtractor circuits. Find out their output equation using any techniques and draw their logical circuit. Form truth table and verify it.

## Half Subtractor

### Truth Table:

A	B	D	B <sub>0</sub>
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

### Equation:

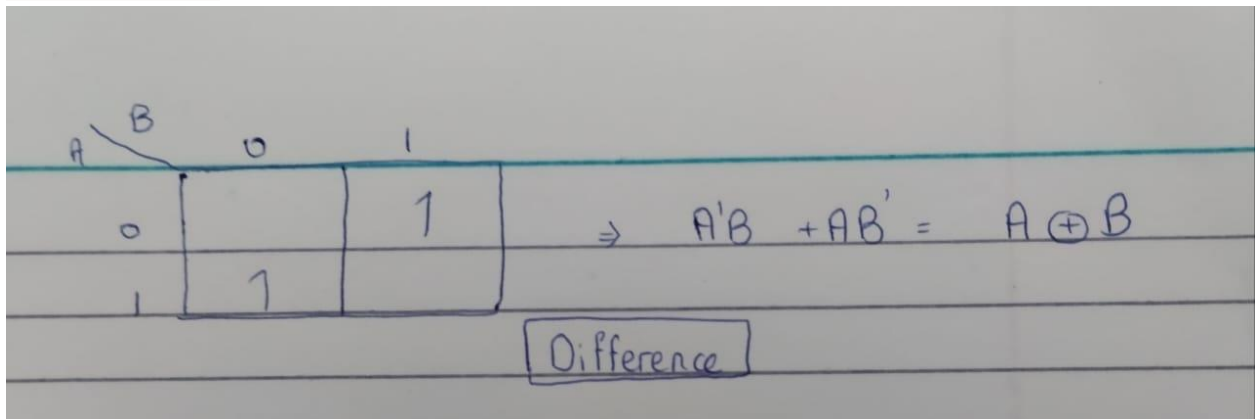


Handwritten truth table for Difference (D):

A \ B	0	1
0		1
1	1	

$\Rightarrow A'B + AB' = A \oplus B$

Difference

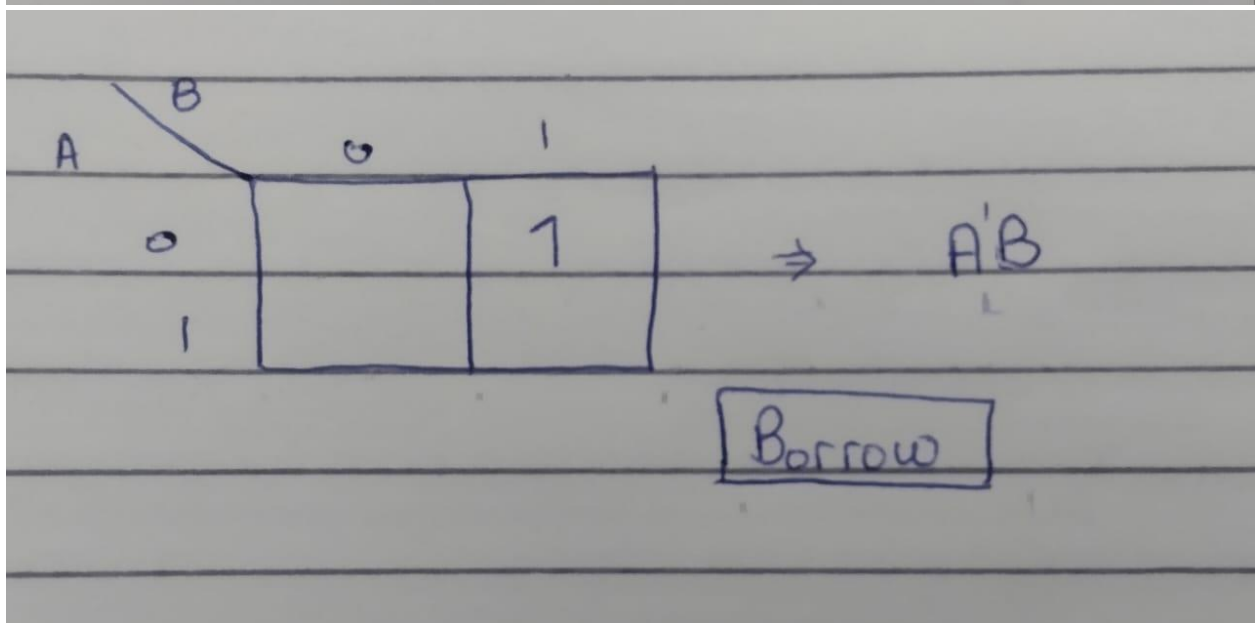


Handwritten truth table for Borrow (B<sub>0</sub>):

A \ B	0	1
0		1
1		



$\Rightarrow A'B$

Borrow

## Circuit:

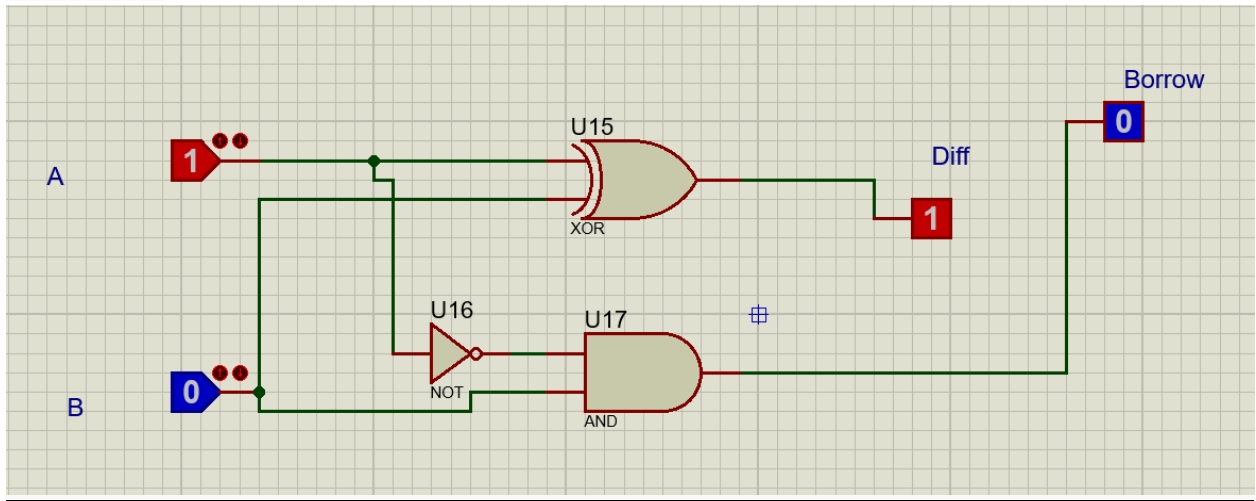

## Working:

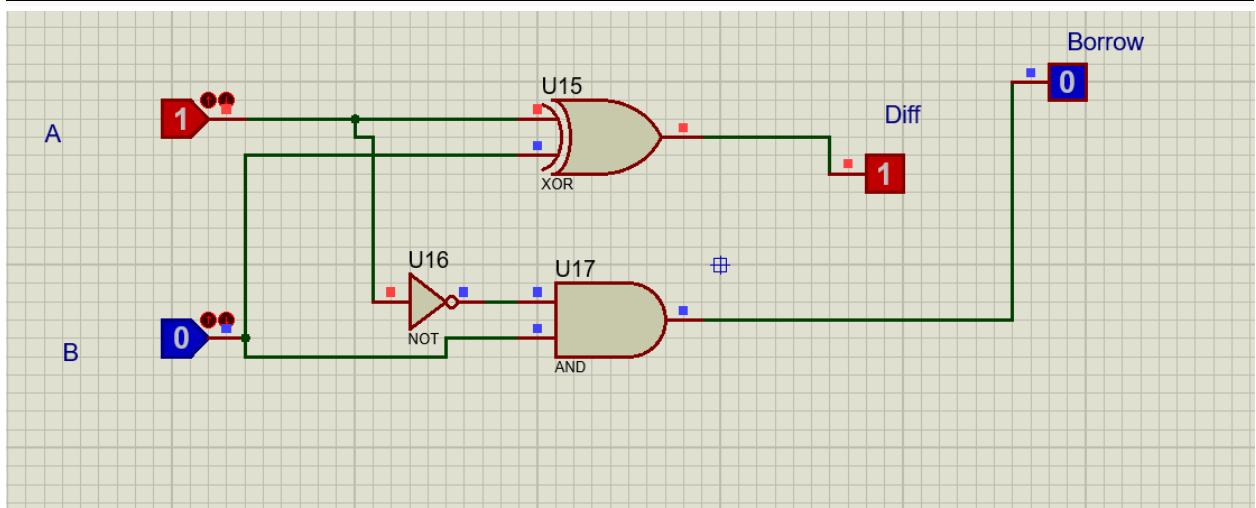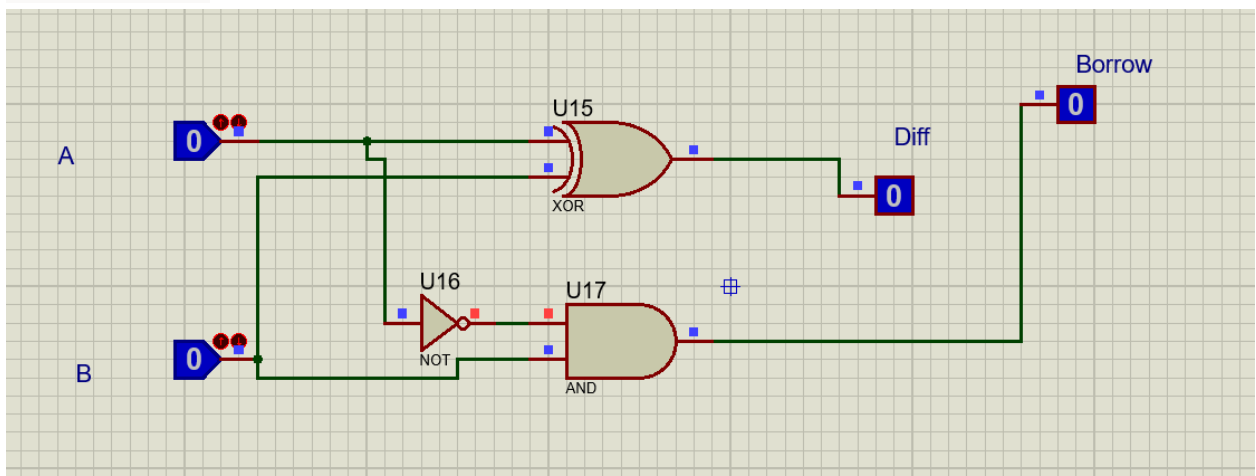




X	Y	Z	Diff	Bor
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

**Equation:**



AB \ C		0	1	$\Rightarrow A'B'C + A'BC' + ABC + AB'C'$ <div>Difference</div>
00			1	
01		1		
11			1	
10		1		

AB \ C		0	1	$\Rightarrow BC' + AC' + AB$
00				
01		1		
11		1	1	
10		1		



## Circuit:

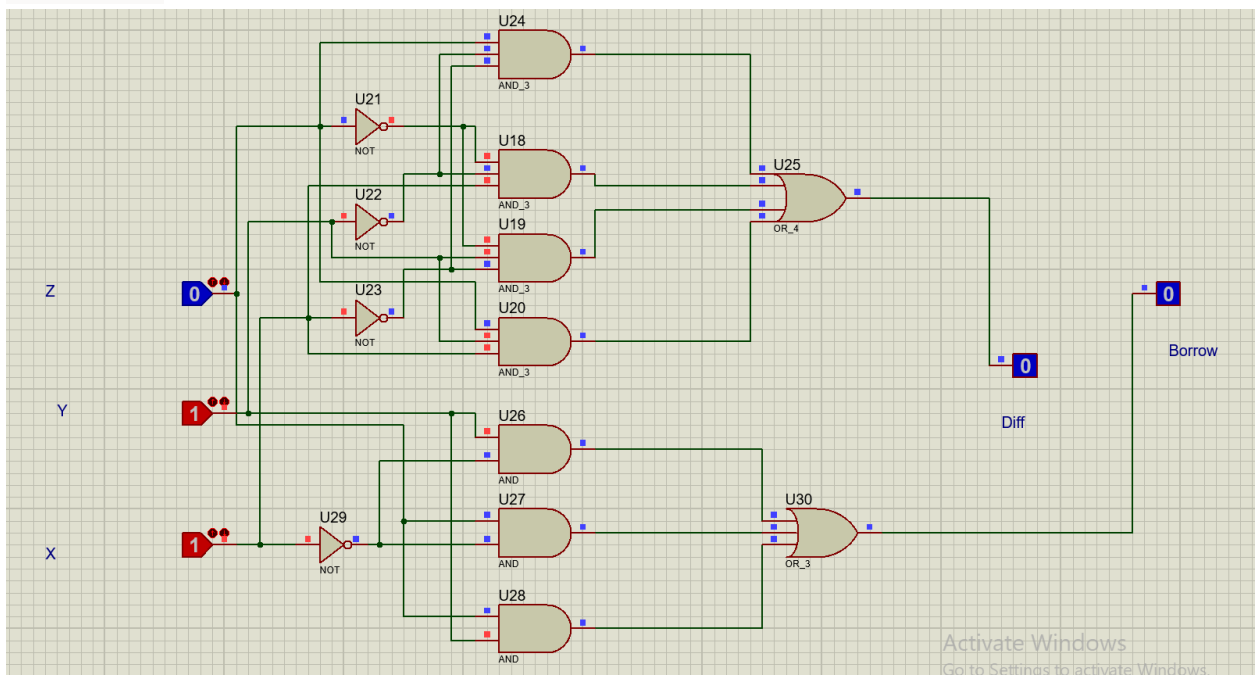

## Working:

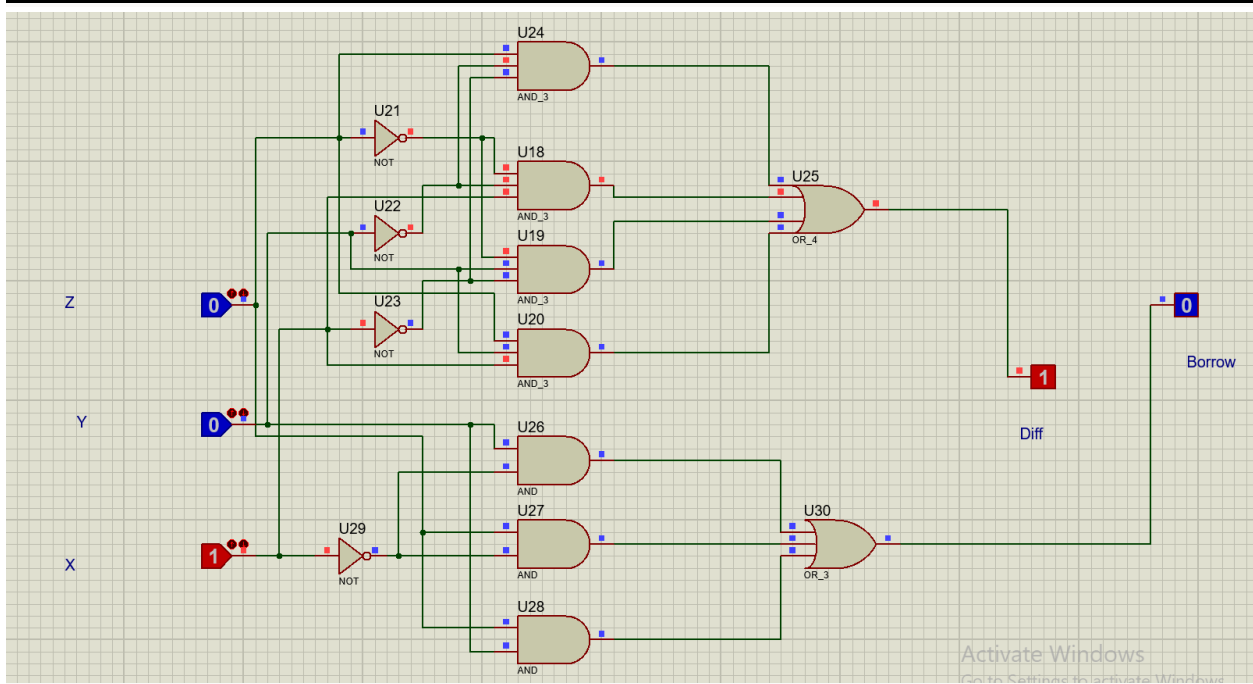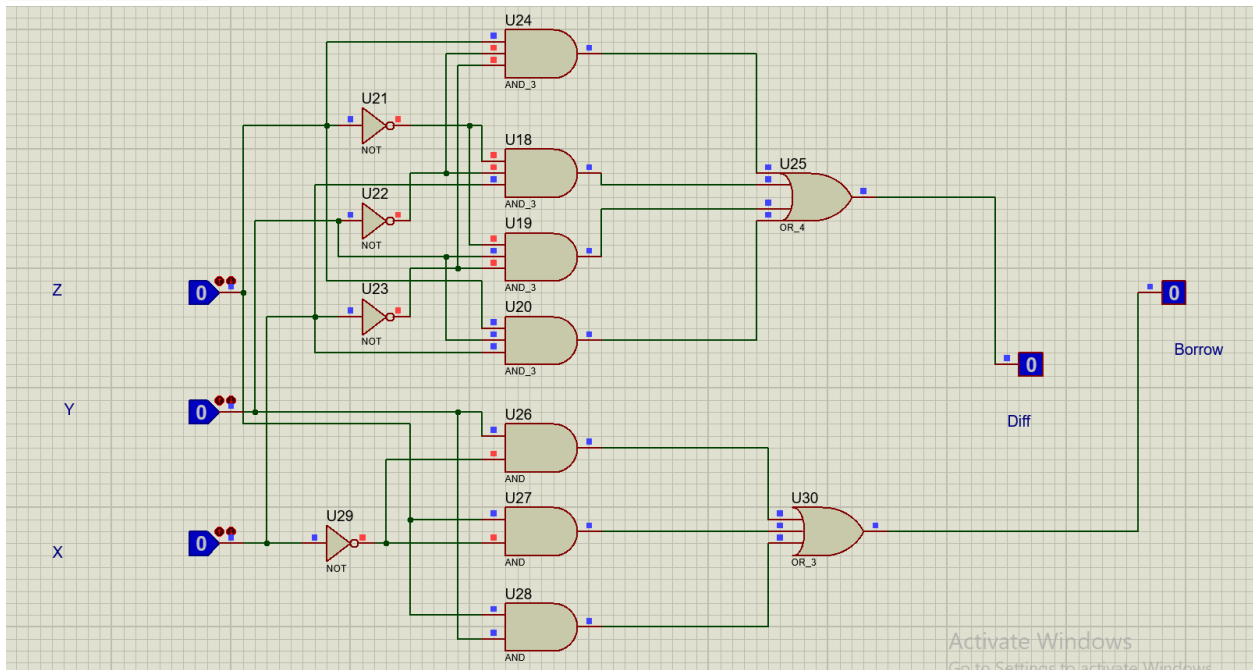



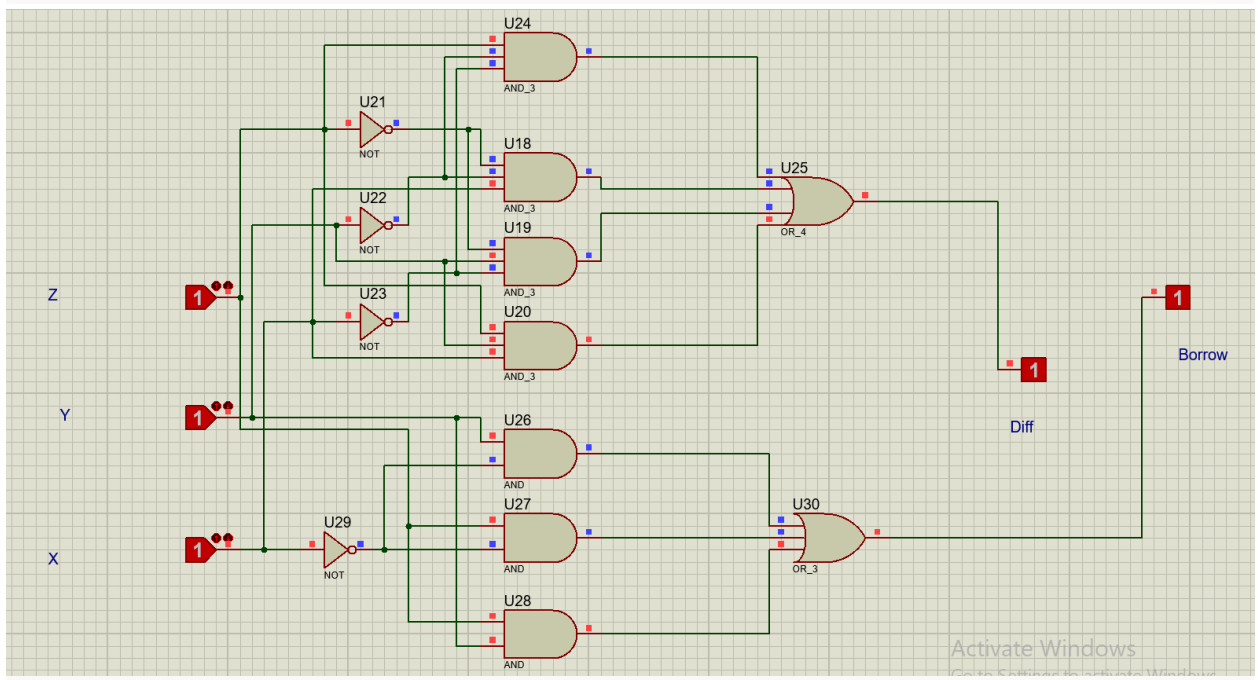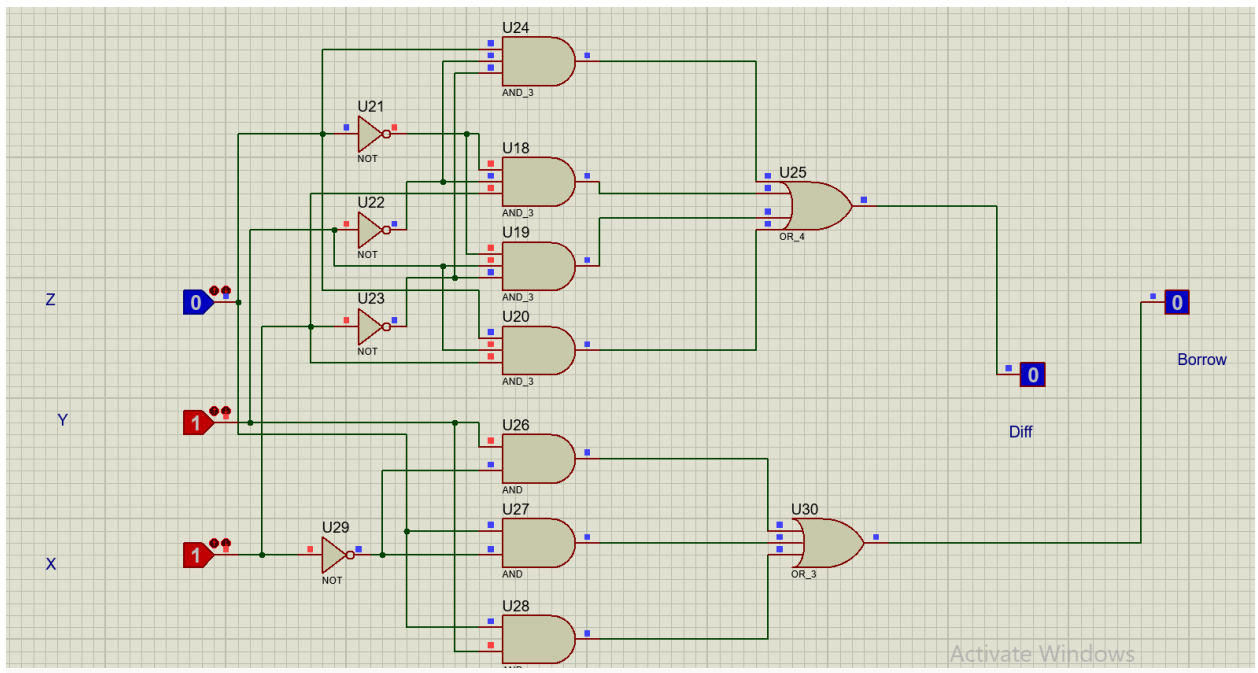

### Task 3:

Implement 4-bit adder, you have to perform addition of following number for input A and B respectively.

6, 7


8, 3

3, 9

11, 4

Without carry input and also with carry input.  
And show carry out results as well.

### Circuit:

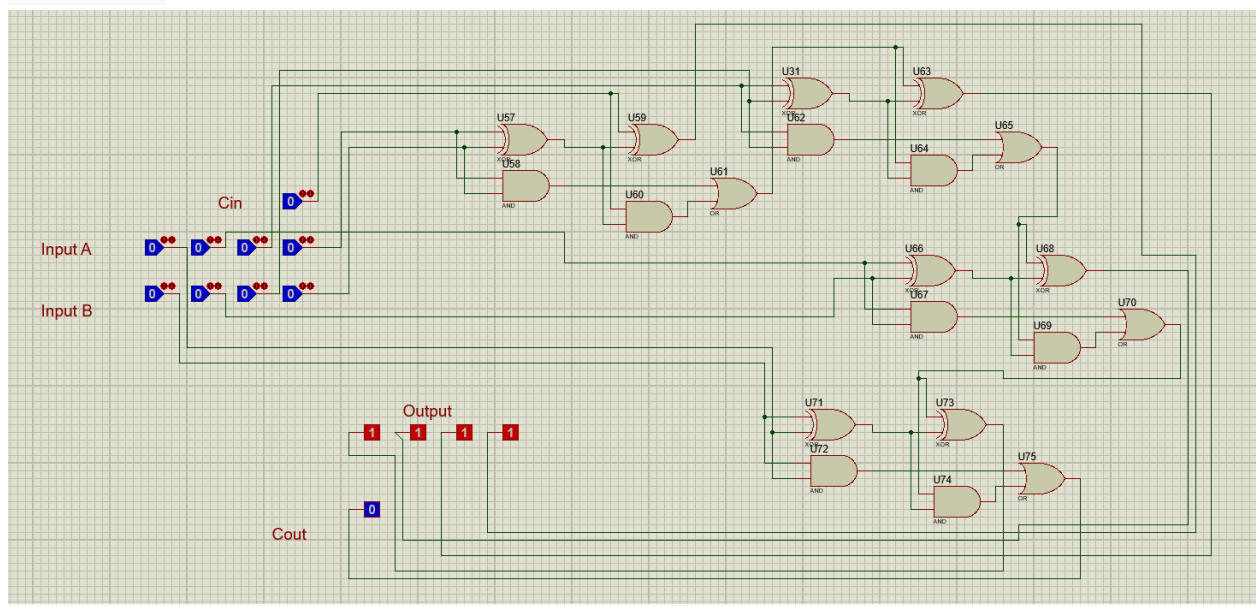

### Working:

1. 6 and 7:

6 = 0110

7 = 0111

6+7 = 13 = 1101

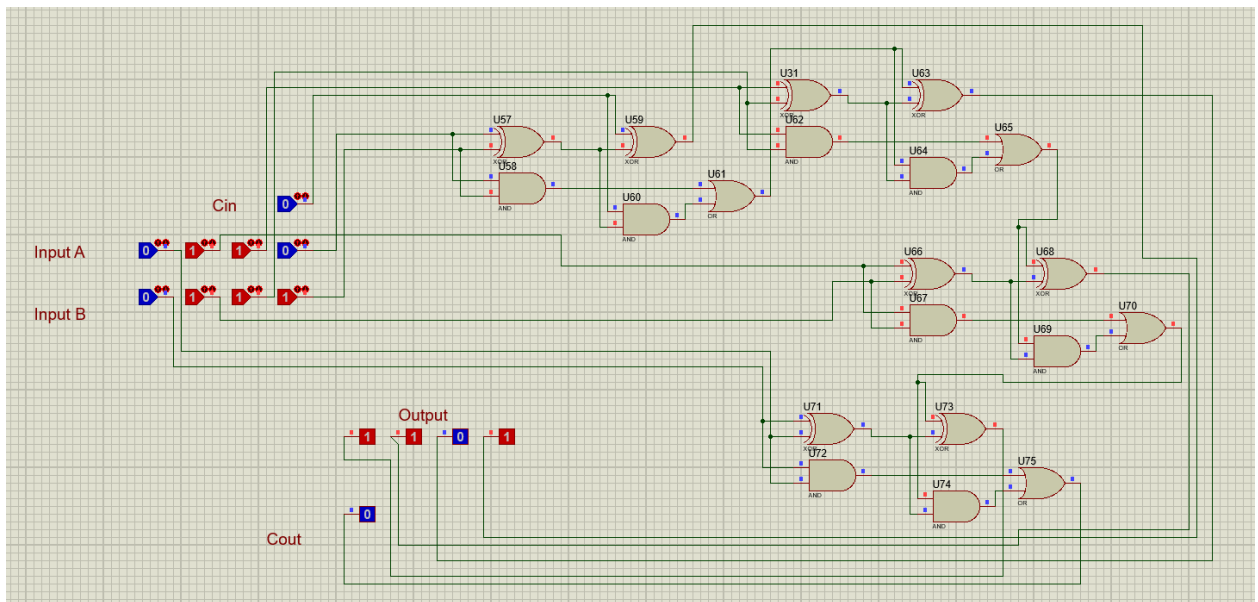


Figure 1: Without Carry bit

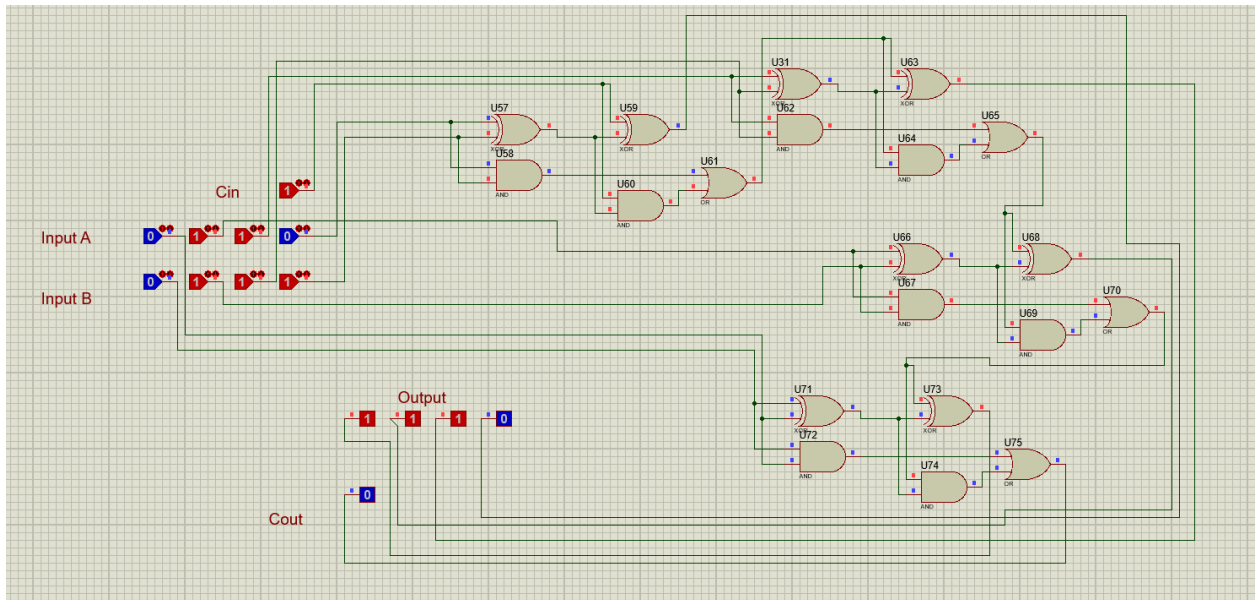


Figure 2: With Carry bit

**2. 8 and 3:**

8 = 1000

3 = 0011

8+3 = 11 = 1011

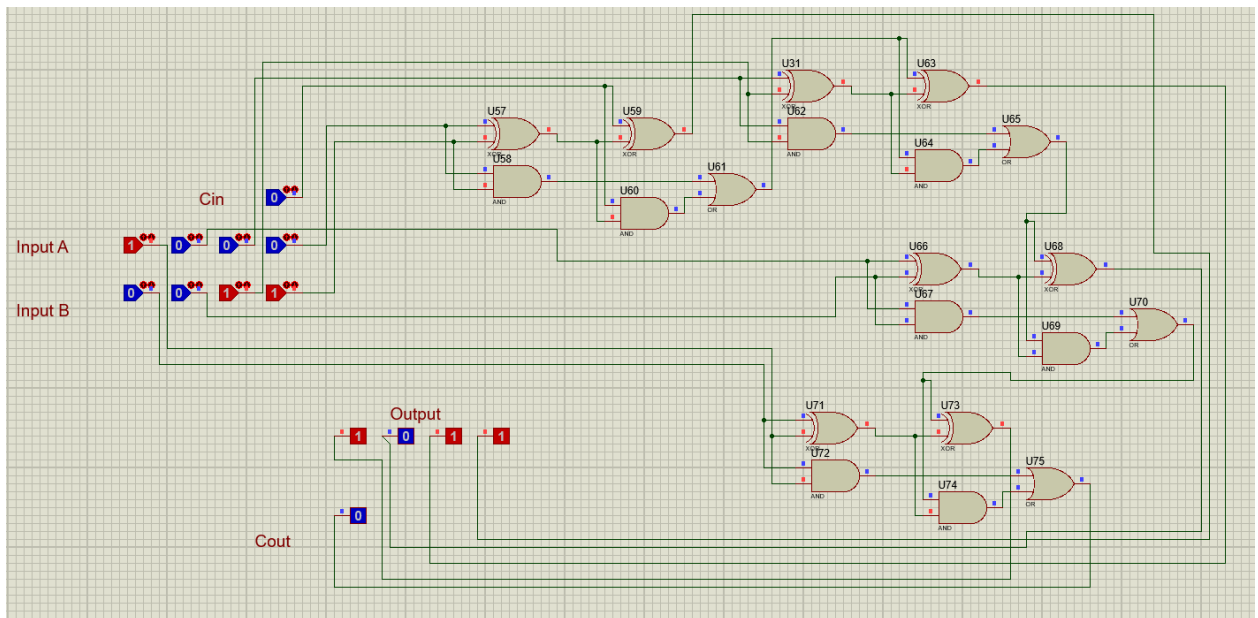


Figure 3: Without Carry bit

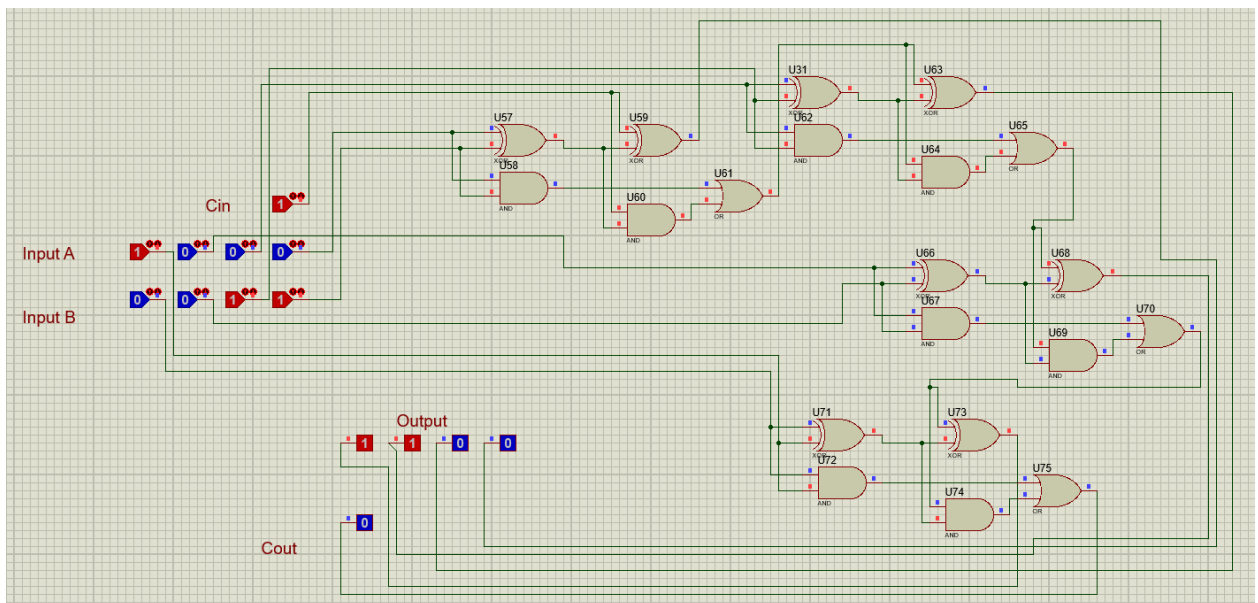


Figure 4: With carry bit

**3. 3 and 9:**

3 = 0011

9 = 1001

3+9 = 12 = 1100

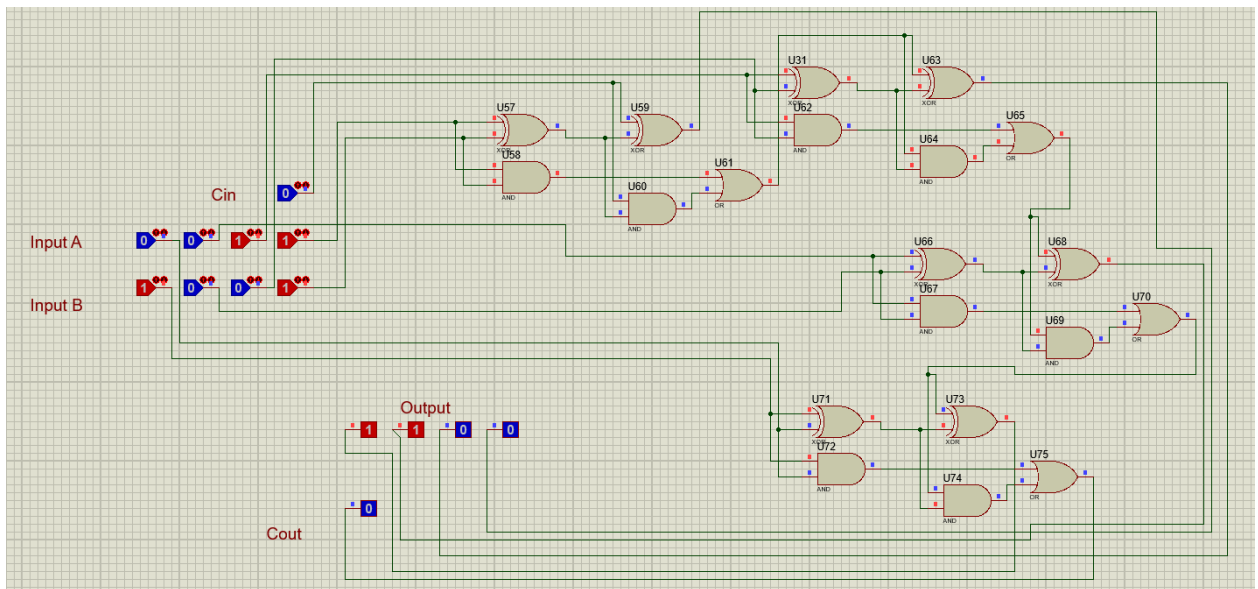


Figure 5: Without carry bit

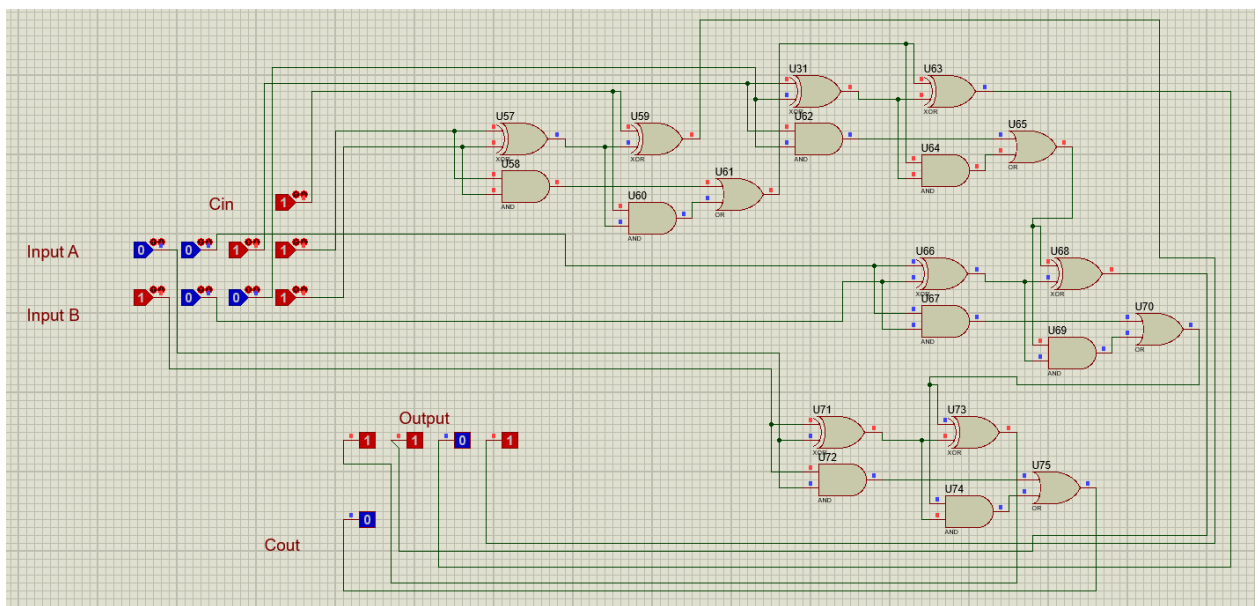


Figure 6: With carry bit

**4. 11 and 4:**  
 11 = 1011  
 4 = 0100  
 11+4 = 15 = 1111

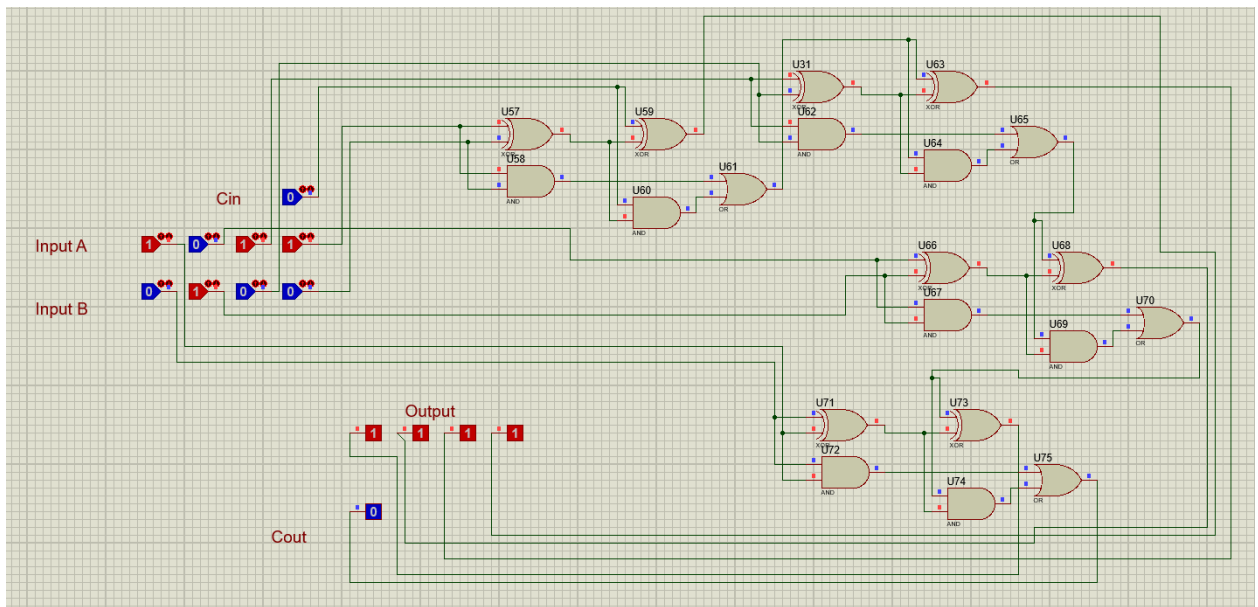


Figure 7: Without carry bit

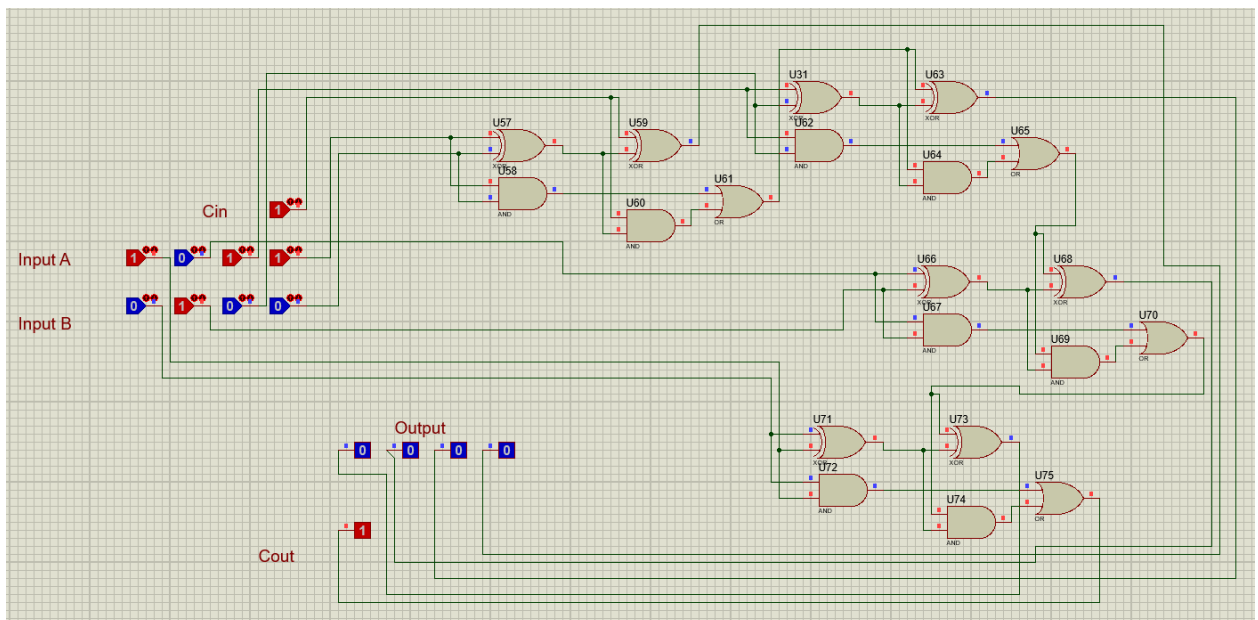


Figure 8: With carry bit

## Task 4:

Implement 4-bit adder subtractor circuit and verify results. You have to verify the following combinations.

0000, 0000


0001, 1000

0010, 0100


1111, 0110

With  $M = 0$  and  $1$ .

Adder Subtractor diagram:

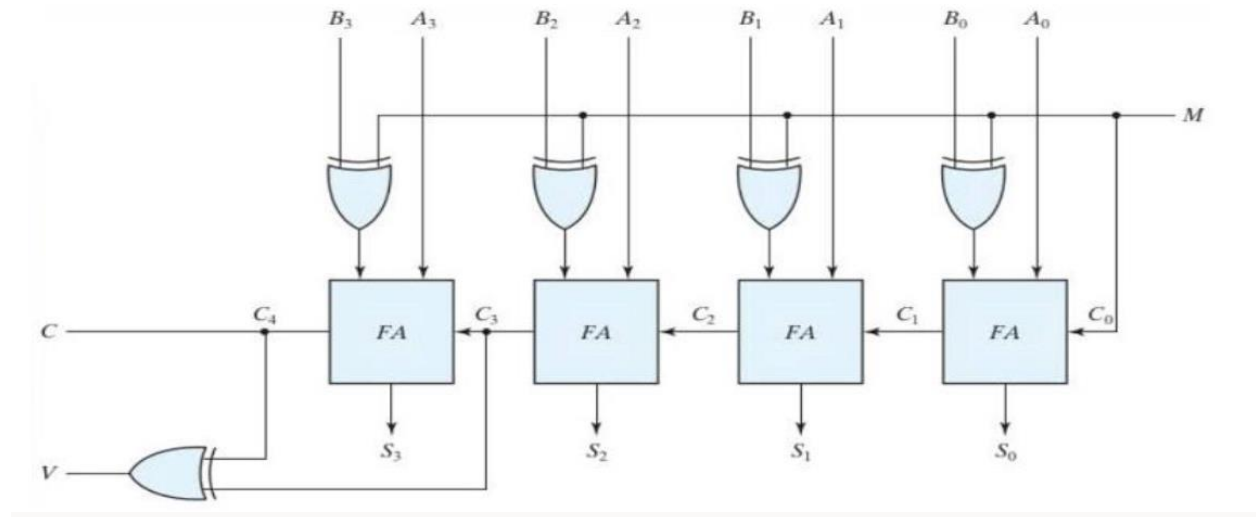

Circuit:

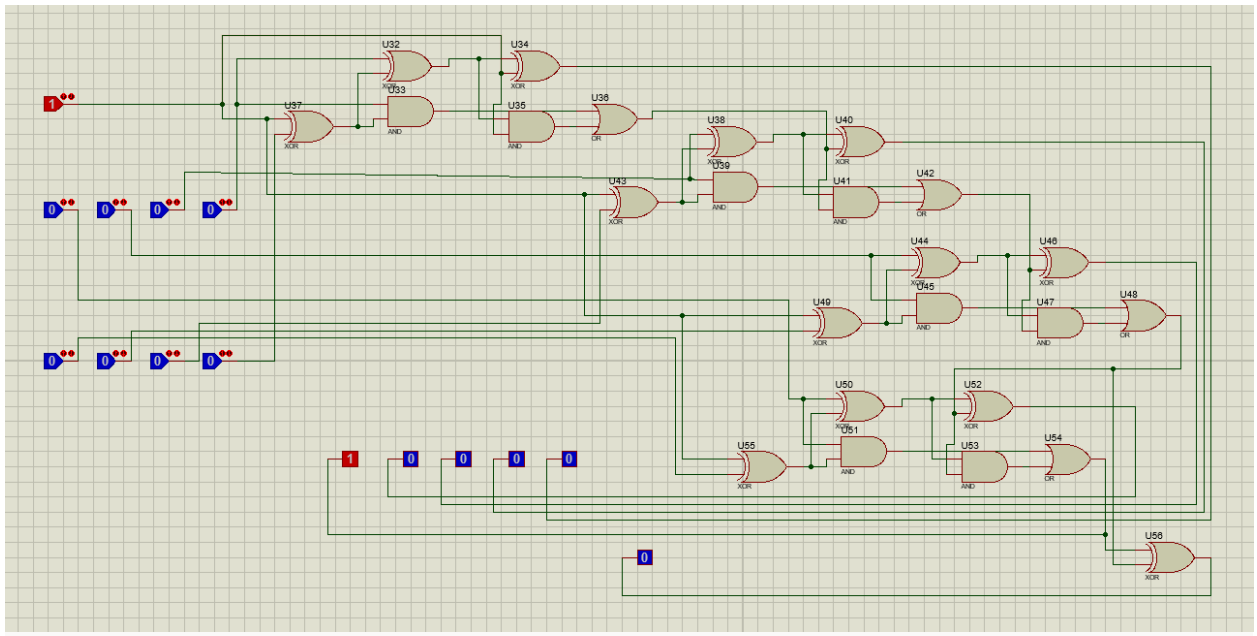


**Working:**

**1. 0000, 0000:**

**M=0 (Addition)**


$$0000 + 0000 = 0000$$

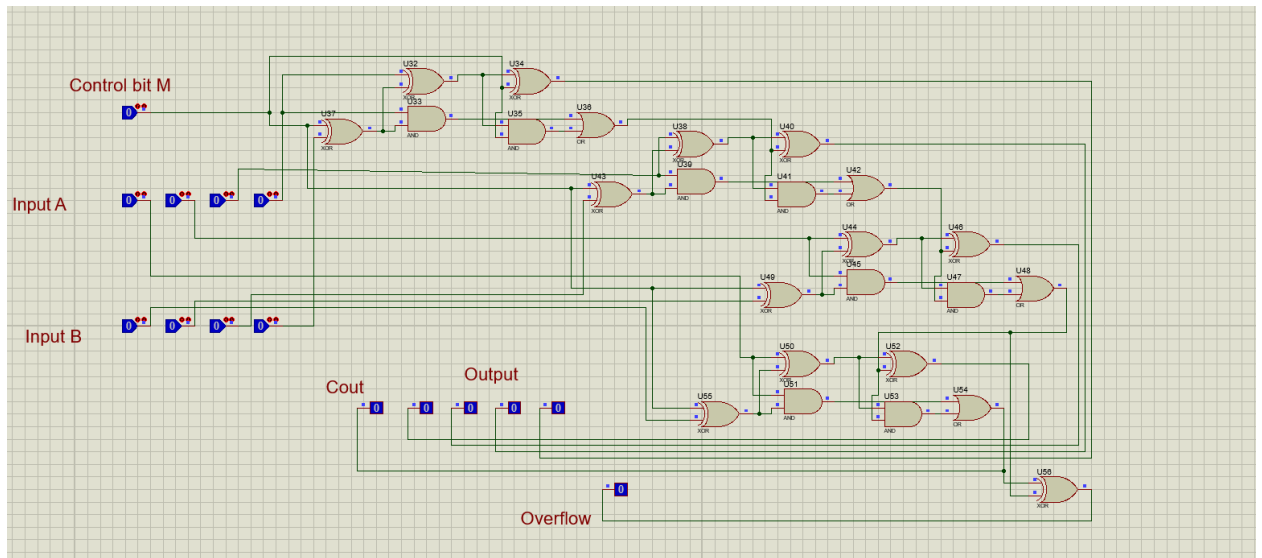

**M=1 (Subtraction)**




$$0000 - 0000 = 0000$$

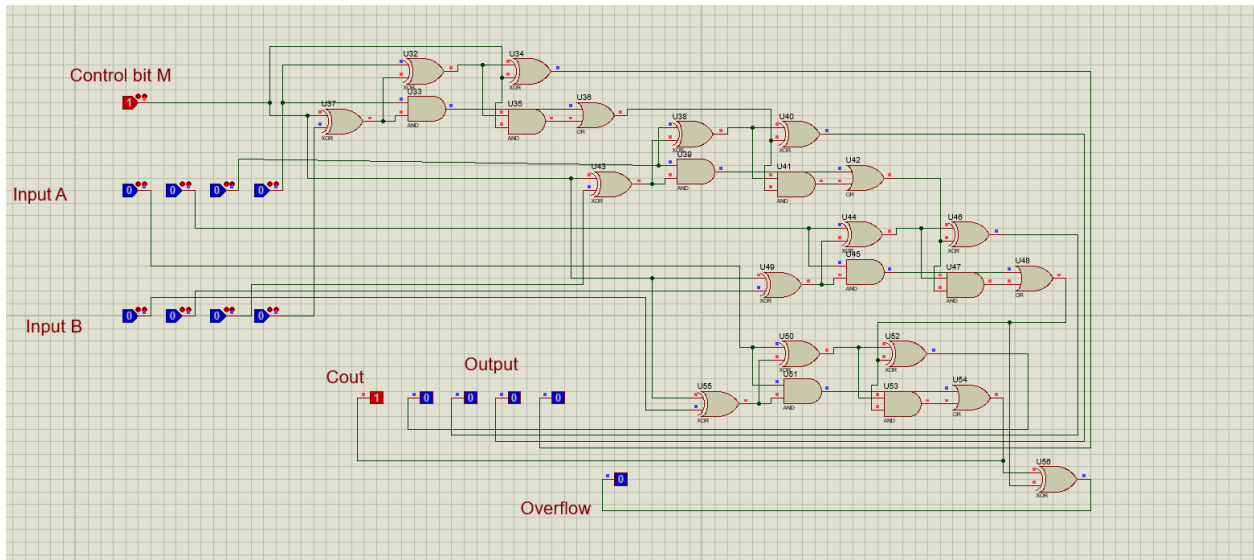

2. 0001, 1000:


**M=0 (Addition)**

$$0001 + 1000 = 1001$$

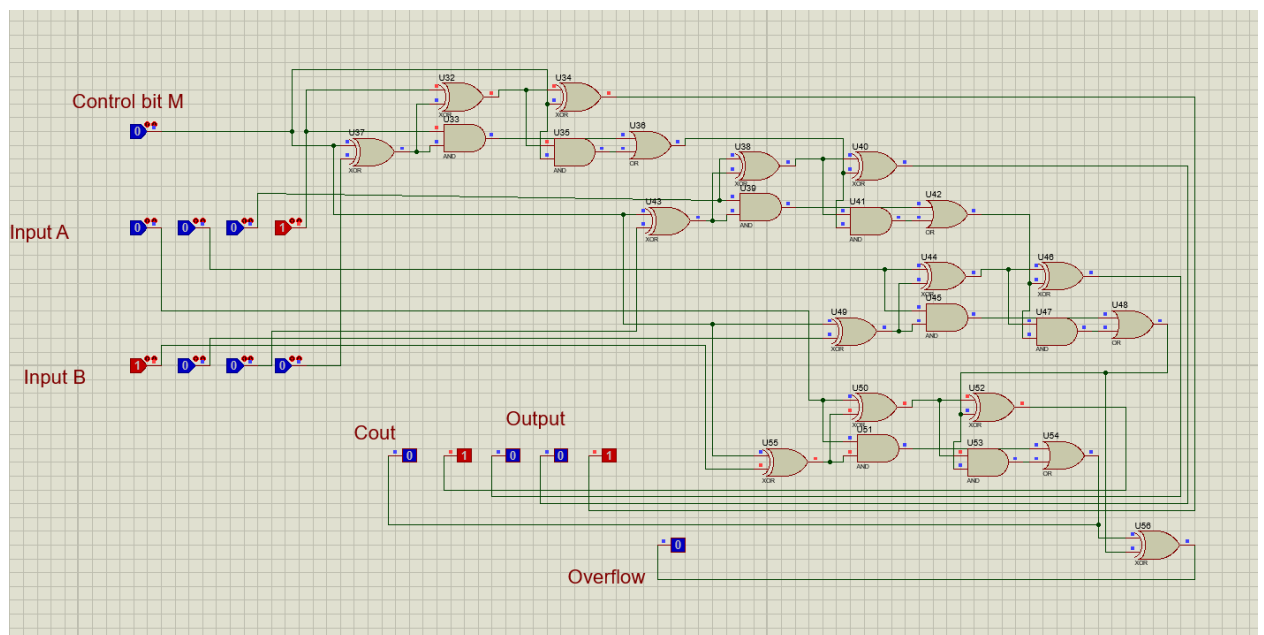

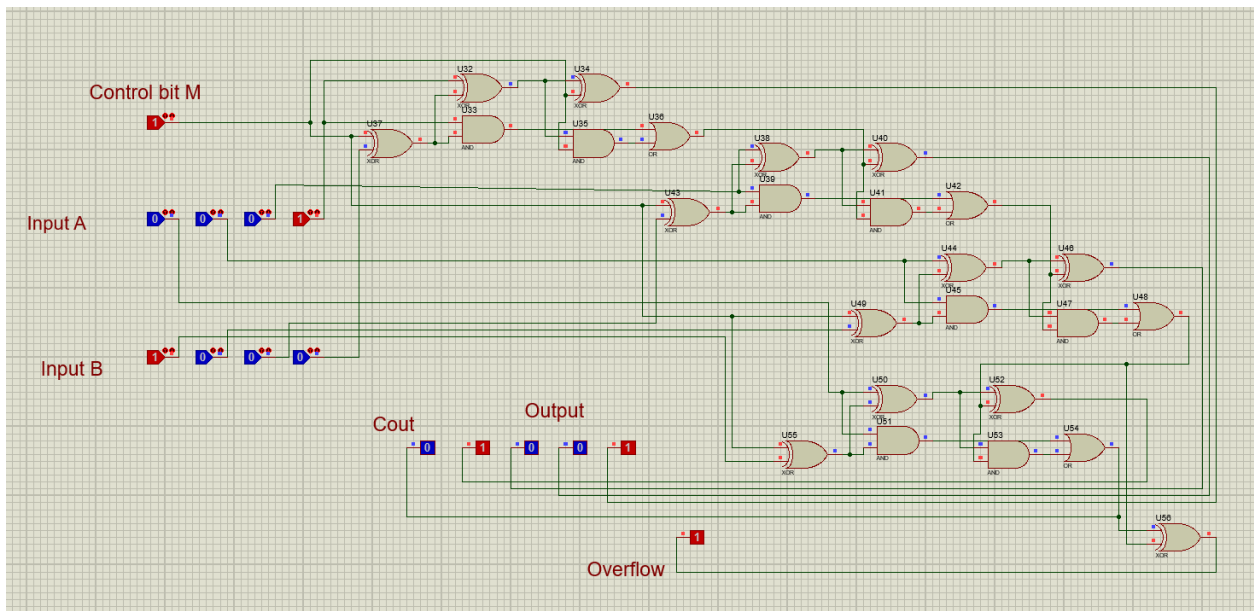**M=1 (Subtraction)**


$$0001 - 1000 = 1001 \text{ with 1 borrow}$$



3. 0010, 0100:


**M=0 (Addition)**

$$0010 + 0100 = 0110$$

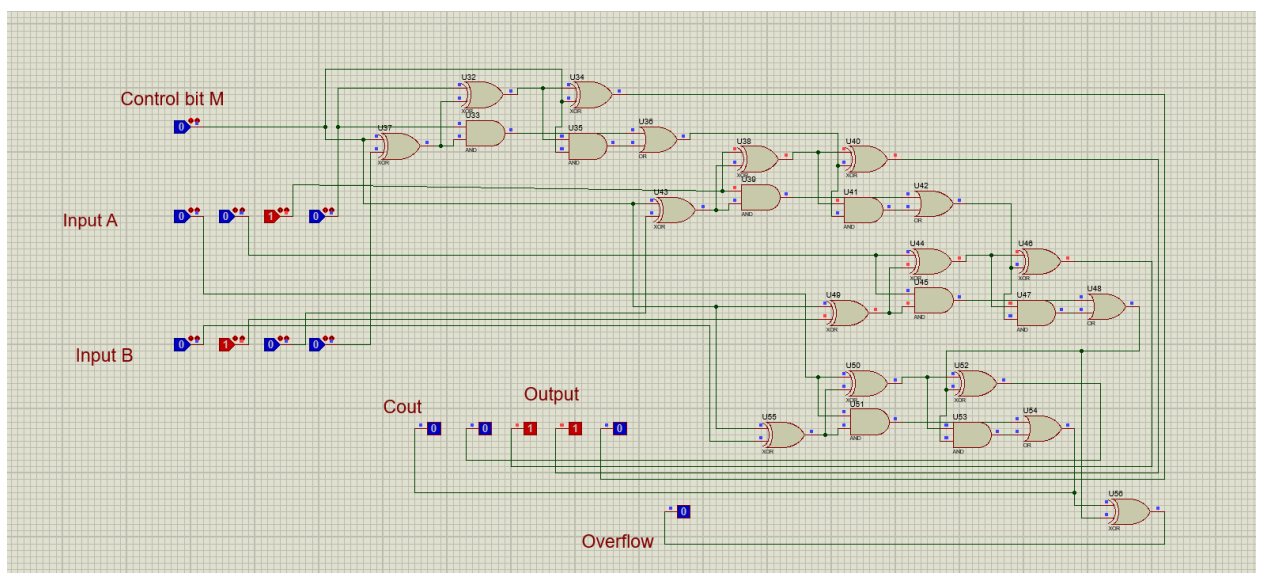

**M=1 (Subtraction)**


$$0010 - 0100 = 1110$$

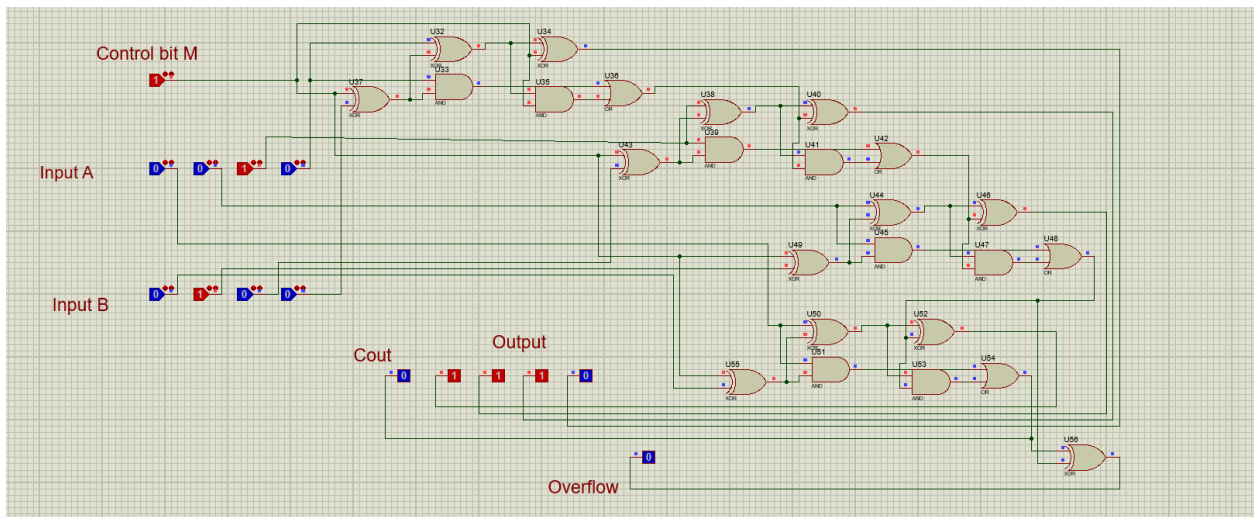

4. 1111, 0110:


**M=0 (Addition)**

1111 + 0110 = 0101 with 1 carry

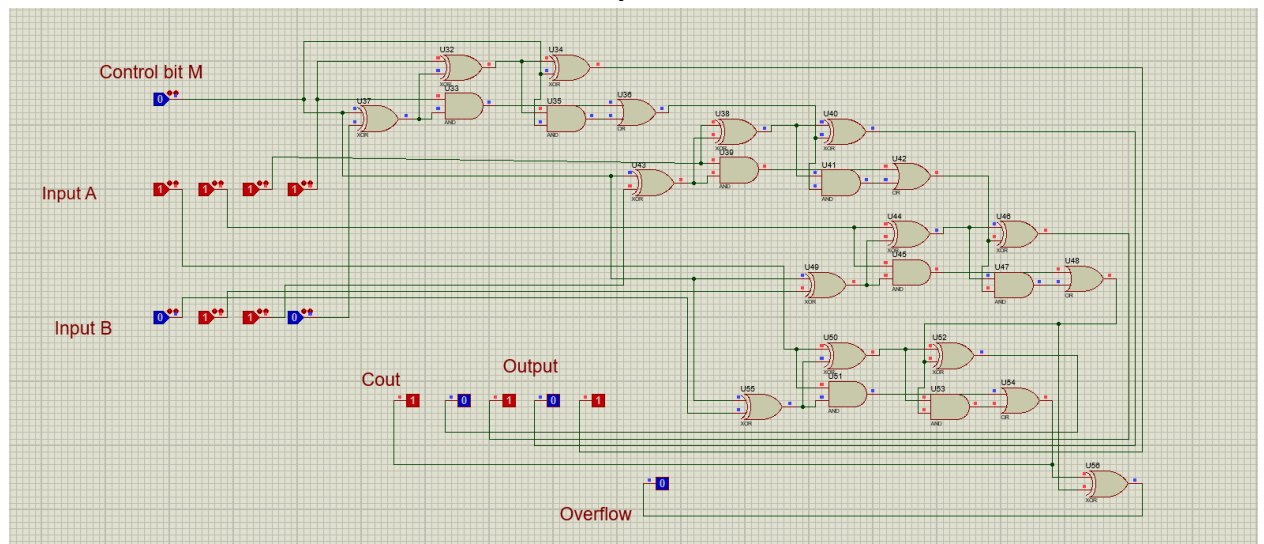

**M=1 (Subtraction)**

1111 - 0110 = 1001

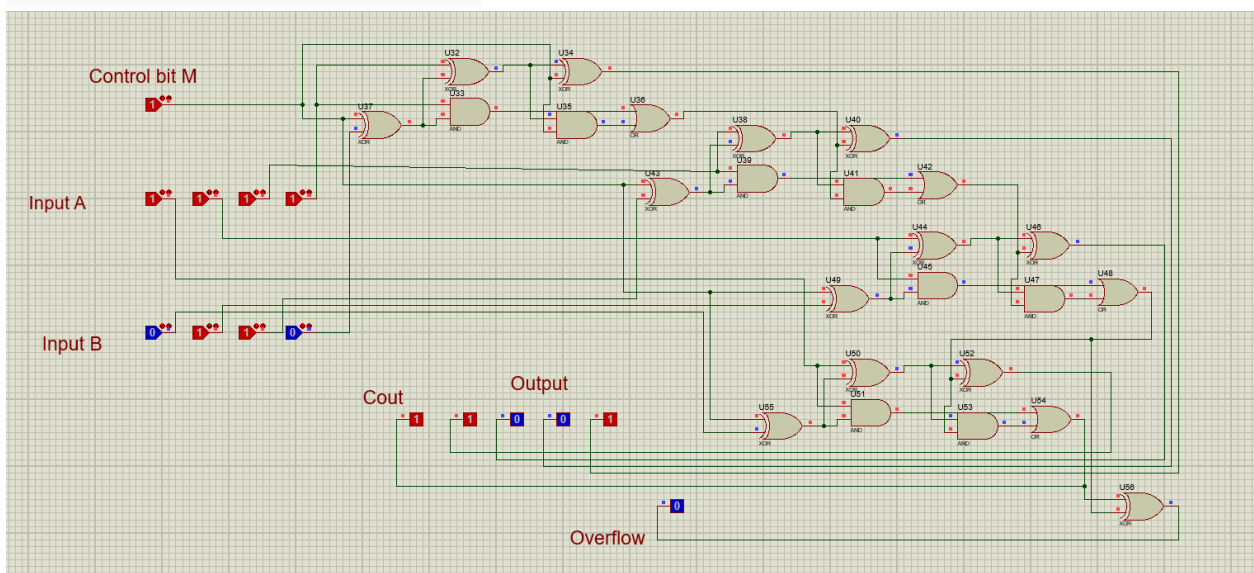

## Conclusion:

In this lab, we have learned how to construct the half adder and full adder circuits, their implementations and their truth tables. We have also learned the same for half and full subtractor circuits, and their implementation.

We have also learned to implement a full adder for any number of bits by making a combinatorial circuit using N number of full adders, to add N number of bits together.

We have also learned to make a Adder-Subtractor circuit, which uses a control bit to both add or subtract based on the control.